

By Sri Arindam Changder\* Department of Physics Raniganj Girls' College

\*email: changderarindam96@gmail.com



This is a little approach to ensure the access of study materials for the Physics (Hons.) students of 2<sup>nd</sup> Semester, Dept. of Physics,RaniganjGirls'College (Aff. To Kazi Nazrul university) during the emergency "COVID-19 pandemic lockdown" period .

The study material is being prepared as per the Syllabus of Kazi Nazrul university.

<u>Course details</u>: This chapter is under the "Core Course-4: Electricity and magnetism".

### <u>Syllabus</u>

Nerwork theorems: Ideal Constantvoltage and constant-current Sources, Network theorems: Thevenin theorem, Norton theorem, Superposition theorem, Reciprocity theorem, Maximum power transfer theorem. Applications to dc circuits.

### <u>Reference</u> :

- 1. A TEXTBOOK OF ELECTRICAL TECHNOLOGY: VOL- I: B.L. THEREJA, A.K. THERAJA
- ELECTRICITY AND MAGNETISM:
   D.CHATTOPADHYAY AND P.C.
   RAKSHIT
- 3. ELECTRICITY AND MAGNETISM:

MAHAJAN AND RANGWALA

## Few important terminologies:

- **1. Circuit:** A circuit is a closed conducting path through which an electric current either flows or is intended flow.
- 2. **Parameters:** The various elements of an electric circuit are called its parameters like resistance, inductance and capacitance.
- **3.** Linear Circuit: A linear circuit is one whose parameters are constant *i.e.* they do not change with voltage or current.
- 4. Non-linear Circuit: It is that circuit whose parameters change with voltage or current.
- 5. **Bilateral Circuit:** A bilateral circuit is one whose properties or characteristics are the same in either direction. The usual transmission line is bilateral, because it can be made to perform its function equally well in either direction.
- 6. Unilateral Circuit: It is that circuit whose properties or characteristics change with the direction of its operation. A diode rectifier is a unilateral circuit, because it cannot perform rectification in both directions.
- 7. Electric Network: A combination of various electric elements, connected in any manner whatsoever, is called an electric network.
- 8. Passive Network: It is one which contains no source of e.m.f. in it.
- 9. Active Network: It is one which contains one or more than one source of e.m.f.
- 10. Node: It is a junction in a circuit where two or more circuit elements are connected together.
- **11. Branch:** It is that part of a network which lies between two junctions.
- **12.** Loop: It is a close path in a circuit in which no element or node is encountered more than once.
- 13. Mesh: It is a loop that contains no other loop within it.

Now, we have to introduce some basic laws to understand the network theorems which are going to be used for the analytical solution of problems related to complex electrical networks.

**Ohm's law:** For a conductor, such as a metal, a linear relationship exists between the potential difference of the two ends of the conductor and the current flowing between them provided the temperature and the other physical conditions remain unchanged. This is the so called **ohm's law**.

For a straight conducting wire of uniform cross-sectional area, if V be the potential difference between any two points of the wire, Ohm's law takes the form:

\_\_\_\_\_

V=IR (1) Where, I is the current flowing through the two points of the wire and R is the proportionality constant, called the resistance of the wire. The resistance has the unit of volt/ampere or ohm  $(\Omega)$  in SI. If 1 is the length and A is the cross-sectional area of the wire, the resistance R is given by,  $\frac{R=\rho l/A}{r}$ 

Where,  $\rho$  is a constant depending on the material of the wire, called the resistivity of the material and has the unit of ohm-meter.



Fig: V-I characteristics for ohmic devices.

Kirchhoff's laws: Kirchhoff's laws offer a convenient expression for the solution of dc circuit problems. These laws can be stated in the following way:

1. Kirchhoff's current law (KCL): The algebraic sum of all the currents at any junction is zero.

If a current flowing towards a junction is taken as positive, a current flowing out of the junction must be taken as negative.



It is a consequence of conservation of charge.

2. **Kirchhoff's voltage law (KVL):** The sum of the IR drops around any loop is equal to the total emf acting in that loop.

From figure, according to 
$$R_3 = E_1 D$$
  
 $KVL$ , we can write,  
 $I_3R_3 + E_1 + I_4R_4 - E_2 + I_1R_1 - I_2R_2 = 0$   
 $or$ ,  $I_1R_1 - I_2R_2 + I_3R_3 + I_4R_4 = E_2 - E_1$   
 $Fig:$  Application of  $KVL$  to a loop.

It is a consequence of conservation of energy.

### **4** <u>Ideal Constant-voltage source and ideal constant-current source</u>:

An ideal voltage source is a voltage generator whose output voltage is independent of the current delivered by the generator. The symbol for an ideal voltage source and its current-voltage characteristics is shown in figure-A.

An ideal voltage source must have zero internal impedance. A practical voltage source always has some internal impedance.

So, a practical voltage source can be represented by an ideal voltage source in series with a resistance or an impedance, which is shown in figure-B.



An ideal current source is a current generator which supplies a current independent of the voltage across the terminals of the current generator. The symbol of an ideal current source and its' current-voltage characteristics is shown in figure-C. An ideal current source must have infinite internal impedance.

A practical current source can be represented by an ideal current source in parallel with an internal impedance as shown in figure-D.



## Metwork theorems:-



$$\begin{array}{c} \cdot \mathbf{I}_{L} = \frac{\sqrt{8}R_{3}}{(R_{1}+R_{3}+r)(R_{2}+R_{3}+R_{4})-R_{3}^{2}} \\ = \frac{\sqrt{8}R_{3}}{(R_{2}+R_{4})(R_{1}+R_{3}+r)+R_{3}(R_{1}+R_{3}+r)-R_{3}^{2}} \\ = \frac{\sqrt{8}R_{3}}{(R_{2}+R_{4})(R_{1}+R_{3}+r)+R_{3}(R_{1}+r)+R_{3}^{2}-R_{3}^{2}} \\ = \frac{\sqrt{8}R_{3}}{(R_{2}+R_{4})(R_{1}+R_{3}+r)+R_{3}(R_{1}+r)} \\ \end{array}$$

$$\begin{array}{c} = \frac{\sqrt{8}R_{3}}{(R_{2}+R_{4})(R_{1}+R_{3}+r)+R_{3}(R_{1}+r)} \\ \end{array}$$

$$\begin{array}{c} = \frac{\sqrt{8}R_{3}}{(R_{2}+R_{4})(R_{1}+R_{3}+r)+R_{3}(R_{1}+r)} \\ \end{array} \\ \begin{array}{c} = \frac{\sqrt{8}R_{3}}{(R_{2}+R_{4})(R_{1}+R_{3}+r)} \\ \end{array} \\ \end{array} \\ \begin{array}{c} = \frac{\sqrt{8}R_{3}}{(R_{1}+R_{3}+r)} \\ \end{array} \\ \end{array} \\ \begin{array}{c} = \frac{\sqrt{8}}{(R_{1}+R_{3}+r)} \\ \end{array} \\ \begin{array}{c} = \frac{\sqrt{8}}{(R_{1}+R_{3}+r)} \\ \end{array} \\ \end{array} \\ \begin{array}{c} = \frac{\sqrt{8}R_{3}}{(R_{1}+R_{3}+r)} \\ \end{array} \\ \end{array} \\ \end{array} \\ \begin{array}{c} = \frac{\sqrt{8}R_{3}}{(R_{1}+R_{3}+r)} \\ \end{array} \\ \end{array} \\ \begin{array}{c} = \frac{\sqrt{8}R_{3}}{(R_{1}+R_{3}+r)} \\ \end{array} \\ \end{array} \\ \end{array} \\ \end{array} \\ \begin{array}{c} = \frac{\sqrt{8}R_{3}}{(R_{1}+R_{$$



*i* rage

# Norton's theorem :-According to this theorem, in a circuit containing linear ohmic rezistances and energy sources, the current flowing through a load resistance is the same as that obtained from a Single current Source IN in parallel with a resistance RN. where, IN is the short-circuit current between the terminal of the network and RN is the resistance measured between the terminals with all the energy sources are replaced by their internal resistances. Proof --To prove this theorem, let us consider the following two port network as shown in fig-I. the set of a set of the From(1) IR+ + IR3-V3 + IT- ILR3=0 =>  $(R_1+R_3+r)I_1 - R_3I_L = V_S - (1)$ and, from loop (2),  $R_2I_1 + R_1I_1 + R_3I_1 - I_1R_3 = 0$ =)  $-R_3I_1 + (R_2 + R_3 + R_4)I_1 = 0$ (R++R3+8) VS  $I_{L} = \frac{\begin{vmatrix} -R_{3} & 0 \end{vmatrix}}{\begin{vmatrix} (R_{1}+R_{3}+r) & -R_{3} \\ -R_{3} & (R_{2}+R_{3}+R_{L}) \end{vmatrix}}$ (R1+R3+8) (R2+R3+R4)

Let us now Solve the problem by applying Norton's theorem. Infig-II. Step-1 the load & has been replaced by a connecting wire (Conducting), which makes the terminals a and b short circuited. Applying KVL, we have,  $R_{11} + R_{3}I_{1} - V_{5} + TI_{1} - I_{N}R_{3} = 0$ =>  $(R_1+R_3+r)I_1 - R_3I_N = V_5 - (4)$ R2IN + R3IN - R3I = 0 = -R<sub>3</sub>I<sub>1</sub> + (R<sub>2</sub>+R<sub>3</sub>)I<sub>N</sub> = 0 - (5) solving these two equation by Cramer's rule, | (Ri+R3+r) vs |  $= \frac{V_{S}R_{3}}{(R_{1}+R_{3}+r)(R_{2}+R_{3})-R_{3}^{2}}$  $I_{N} = \frac{|-R_{3} 0|}{|(R_{1}+R_{3}+r) - R_{3}|}$ (6)  $-R_3$  (R2+R3) Step-II To find Norton's resistance RN, we consider fig-III, where, the Source has been replaced by it's internal resistance.  $R_{N} = R_{2} + R_{3}(R_{1} + r)$  $= R_{N} = \frac{R_{2} + \frac{R_{3}(R_{1}+r)}{(R_{3}+R_{1}+r)}}{(R_{3}+R_{1}+r)} + R_{3}(R_{1}+r)} - (7)$  $(R_3+R_1+r)$ Step-I Let us now Connect the load resistance RL and the Norton's equivalent crouit is as shown in fig-I. voltage across RN & RL in parallel, V= IN . RNKL (RN+RL) : Current through RL,  $\frac{Fig-IV}{Fig-IV} \\ \frac{Fig-IV}{(R_3+R_1+r)+R_3(R_1+r)} \\ (R_3+R_1+r)$  $I_{L} = \frac{V}{R_{L}} = \frac{I_{N}R_{N}}{(R_{N} + R_{L})}$   $\therefore I_{L} = \frac{V_{S}R_{3}}{\{(R_{1} + R_{3} + r)(R_{2} + R_{3}) - R_{3}^{2}\}} \times \frac{1}{2}$ (RN+RL

$$I_{L} = \frac{V_{S}R_{3} \left\{ k_{2}(R_{3}+R_{4}+r) + R_{3}(R_{4}+r) \right\}}{\left\{ (R_{4}+R_{3}+r)(R_{2}+R_{3}) - R_{3}^{2} \right\} \cdot \left( R_{3}+R_{4}+r) + R_{3}(R_{4}+R_{3}+r) - R_{3}^{2} \right\}} = \frac{V_{3}R_{3} \left\{ k_{2}(R_{3}+R_{4}+r) + R_{3}(R_{4}+R_{3}+r) - R_{3}^{2} \right\}}{\left\{ (R_{4}+R_{3}+r)(R_{2}+R_{3}) - R_{3}^{2} \right\} \left\{ (R_{2}+R_{4})(R_{3}+R_{4}+r) + R_{3}(R_{4}+r) + R_{3}(R_{4}+R_{3}+r) - R_{3}^{2} \right\}$$

$$= \frac{V_{S}R_{3}}{(R_{4}+R_{3}+r)(R_{2}+R_{3}) - R_{3}^{2} \right\} \left\{ (R_{2}+R_{4})(R_{4}+R_{3}+r) - R_{3}^{2} - R_{3}^{2} \right\}$$

$$= \frac{V_{S}R_{3}}{(R_{4}+R_{3}+r)(R_{2}+R_{3}) - R_{3}^{2} \right\} \left\{ (R_{4}+R_{3}+r) - R_{3}^{2} - R_{3}^{2} \right\}$$

$$= \frac{V_{S}R_{3}}{(R_{4}+R_{3}+r)(R_{2}+R_{3}) - R_{3}^{2} - R_{3}^{2} \right\}$$

$$= \frac{V_{S}R_{3}}{(R_{4}+R_{3}+r)(R_{2}+R_{3}) - R_{3}^{2} - R_{3}^{2} - R_{3}^{2} - R_{3}^{2} - R_{3}^{2}$$

$$= \frac{V_{S}R_{3}}{(R_{4}+R_{3}+r)(R_{2}+R_{3}) - R_{3}^{2} -$$



$$\begin{array}{l} \text{Abplying } \text{KVL in fig=I}, \\ \text{Ri}i' + \text{Rs}i'_{1} + \text{V}_{1} + \text{r}_{1}i'_{1} + \text{Rs}i'_{2} &= 0 \\ \Rightarrow (\text{R}_{1} + \text{R}_{3} + \text{r}_{1})i'_{1} + \text{Rs}i'_{2} &= \text{V}_{1} - --(4) \\ \text{Rs}i'_{2} + \text{Rs}i'_{2} + \text{r}_{2}i'_{2} + \text{Rs}i'_{1} &= 0 \\ \Rightarrow \text{Rs}i'_{1} + (\text{R}_{2} + \text{R}_{3} + \text{r}_{2})i'_{2} &= 0 - --(5) \\ \text{Solving (4) and (5) by cramer's rule,} \\ i''_{1} &= \frac{V_{1} \left( \text{R}_{2} + \text{R}_{3} + \text{r}_{2} \right) }{\left( \text{R}_{1} + \text{R}_{3} + \text{r}_{1} \right) \text{R}_{3}} \\ \text{Rs} & (\text{R}_{2} + \text{R}_{3} + \text{r}_{2}) \\ \hline \text{OT. } i'_{1} &= \frac{V_{1} \left( \text{R}_{2} + \text{R}_{3} + \text{r}_{2} \right) }{\left( \text{R}_{1} + \text{R}_{3} + \text{r}_{1} \right) \left( \text{R}_{2} + \text{R}_{3} + \text{r}_{2} \right) - \text{Rs}^{2}} - -(6) \\ \text{Also, using KVL in fig=EII,} \\ \text{Ri}i'' + \text{Rs}i'' + \text{r}_{1}i'' + \text{Rs}i'' &= 0 \\ \Rightarrow (\text{R}_{1} + \text{R}_{3} + \text{r}_{1})i'' + \text{Rs}i'' &= 0 \\ \Rightarrow (\text{R}_{1} + \text{R}_{3} + \text{r}_{1})i'' + \text{Rs}i'' &= 0 \\ \Rightarrow \text{Rs}i'' + (\text{R}_{2} + \text{R}_{3} + \text{r}_{2})i'' &= \text{V}_{2} - -(7) \\ \text{R}_{2}i'' + \text{Rs}i''' + (\text{R}_{2} + \text{R}_{3} + \text{r}_{2})i'' &= \text{V}_{2} - -(8) \\ \text{Solving (7) and (8) by Cramer's rule,} \\ i''' &= \frac{\left( \begin{array}{c} 0 & \text{R}_{3} \\ \text{V}_{2} & (\text{R}_{2} + \text{R}_{3} + \text{r}_{2}) \\ \frac{1}{(\text{R}_{1} + \text{R}_{3} + \text{r}_{1})} \text{R}_{3} \\ \text{R}_{3} & (\text{R}_{2} + \text{R}_{3} + \text{r}_{2}) \end{array} \right) = \frac{-\text{V}_{2} \text{R}_{3} \\ \frac{1}{(\text{R}_{1} + \text{R}_{3} + \text{r}_{1}) \text{R}_{3}}{(\text{R}_{2} + \text{R}_{3} + \text{r}_{2})} = \frac{-\text{V}_{2} \text{R}_{3} \\ - -\text{R}_{3}^{2} \left( \text{q} \right) \end{array}$$

**12 |** Page

From (3),
$(R_2+R_3+r_2)V_1 - R_3V_2$
$(R_1+R_3+r_1)(R_2+R_3+r_2)-R_3^2$
$\sigma r, \hat{\iota}_1 = \frac{V_1(R_2 + R_3 + r_2)}{V_1(R_2 + R_3 + r_2)} + (-R_3 V_2)$
$(R_1+R_3+\gamma_1)(R_2+R_3+\gamma_2)(R_1+R_3+\gamma_1)(R_2+R_3+\gamma_2)-R_3^2$
or, i1 = i1 + i1" (From equations () and ())
Similarly, if we evaluate the values of iz, i' and i''.
then we must have, $i_2 = i_2' + i_2''$
# Reciprocity theorem :-
It states that, in any linear network Containing
ofmic resistances and an energy source, the current
in one loop when the enf acts in the other when the same
ent acts in the former.
Proof:- P. P.
Battery of voltage vo is placed minimum
in the 1st loop. Vat PI, 3R3 LISRL
Applying KVL in the 1st loop,
$I_1R_1 + I_1R_3 - V_6 - I_2R_3 = 0$
=> $I_1(R_1+R_3) - I_2R_3 = V_R_1 + (1)$
and, applying KUL in the 2nd Loop,
$R_2I_2 + R_1I_2 + R_3I_2 - R_3I_1 = 0$
$\Rightarrow -R_3I_1 + (R_2 + R_3 + R_L)I_2 = 0 - (2)$





or, RL = Rg \_\_\_\_ (3) Thus, in a resistive circuit, if the load reasistance is varied, maximum power is absorbed by the load resistance when the load rearstable is equal to the Source resistance. This is known as the maximum power transfer theorem.

# **4** <u>Applications of dc circuits</u>:-

There are widespread applications of dc circuits in the modern era of science and technology. Some of them are discussed in the following-

- 1. DC circuits are commonly found in low voltage applications, especially where these are powered by batteries or solar power systems used in domestic and commercial buildings.
- 2. Most electronic circuits require a DC power supply.
- 3. Most automotive applications use DC. An automotive battery provides power for engine starting, lighting, and ignition system.
- 4. Several dc circuits are used in telecommunication systems.

\*\*\* There may be some unintentional mistakes, if any, students are requested to address me those mistakes through the given email address.

\*\*\* To enhance the analytical handling capacity, students are advised to solve a lot of problems on "Network theorem", highly available on the examples and exercises of the reference books.